



The logic block shown has an output F given by _____

1. $A + B$
2. $A.\bar{B}$
3. $A + \bar{B}$
4. \bar{B}